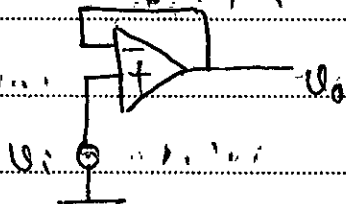
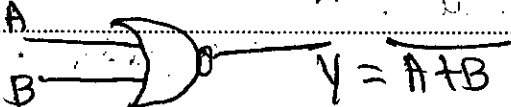




GOVERNMENT OF KARNATAKA
KARNATAKA STATE PRE-UNIVERSITY EDUCATION EXAMINATION BOARD
II YEAR PUC EXAMINATION
SCHEME OF VALUATION OS
 2015

Subject Code : 40

Subject : ELECTRONICS

Qn. No.		Marks
	PART - A	
1.	Emitter region	1
2.	CB Amplifier	1
3.	A feedback in which a part of the output feedback to the input out of phase with it is called negative feedback.	1
4.		1
5.	180° phase shift	
6.	Skip distance is defined as the minimum distance between transmitting antenna and first receiving antenna (station) measured along the surface of Earth after the reflection from the ionosphere.	1
7.	$m_a = 0.8$	1
8.	(1000 000) 10^6	1
9.		1

Qn. No.		Marks
10.	Code division multiple access. PART-B	1
11.	Q-point is the intersection point of the DC load line and the output characteristic of a transistor: $Q(V_{CEQ}, I_{CQ})$	1
12.	$\beta = \frac{I_C}{I_B} \Rightarrow I_C = \beta I_B = 150 \times 10 \times 10^{-6} = 1.5 \text{ mA}$	1
	$I_E = I_C + I_B = 1.5 \text{ mA} + 0.15 \text{ mA} = (1.5 + 0.15) \text{ mA} = 1.65 \text{ mA}$	1
	Ans: $I_C = 1.5 \text{ mA}, I_E = 1.65 \text{ mA}$	
13.	<ul style="list-style-type: none"> a) Frequency bandwidth increases. b) Gain will be stabilized. c) Noise and distortion will be reduced. d) Input impedance increases. e) output impedance decreases. 	2
14.	$A_f = \frac{A}{1 + A\beta}$ $A_f = \frac{100}{1 + 100 \times 0.1} = \frac{100}{11} = 9.091$ <div style="border: 1px solid black; display: inline-block; padding: 2px;">$A_f = 9.091$</div>	1
15.	<ul style="list-style-type: none"> a) voltage gain is $-\infty$ b) input impedance is ∞ c) output impedance is 0 d) CMRR is ∞ e) Frequency bandwidth is ∞ 	2

Qn. No.		Marks		
16	$A_v = -\left(\frac{R_f}{R_i}\right) = -\frac{10 \times 10^3}{2 \times 10^3} \Rightarrow A_v = -5$	1		
	$V_o = I_L R_L = A_v \cdot V_i = -5 \times 0.5 = -2.5 \text{ V}$ <div style="border: 1px solid black; padding: 2px; display: inline-block;"> $V_o = -2.5 \text{ V}$ </div>	1		
17	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%; padding: 5px;"> <p style="text-align: center;">sky wave</p> <p>wave which is travelling to the receiving antenna directly or due to reflection by the ionosphere.</p> </td> <td style="width: 50%; padding: 5px;"> <p style="text-align: center;">ground wave</p> <p>wave which travels directly or by the reflection from the Earth reaches the receiving antenna.</p> </td> </tr> </table>	<p style="text-align: center;">sky wave</p> <p>wave which is travelling to the receiving antenna directly or due to reflection by the ionosphere.</p>	<p style="text-align: center;">ground wave</p> <p>wave which travels directly or by the reflection from the Earth reaches the receiving antenna.</p>	2
<p style="text-align: center;">sky wave</p> <p>wave which is travelling to the receiving antenna directly or due to reflection by the ionosphere.</p>	<p style="text-align: center;">ground wave</p> <p>wave which travels directly or by the reflection from the Earth reaches the receiving antenna.</p>			
18	<p>XNOR gate is a logic gate its output is high when all the inputs are low or even number of inputs are in high state.</p> <p>Using only NAND gates, all the logic gates can be constructed. Hence NAND is called universal gate.</p>	2		
19	$Y = A + \overline{B}C$ $= \overline{A}(B + \overline{B})(C + \overline{C}) + \overline{B}C(A + \overline{A})$ $= \overline{A}BC + \overline{A}B\overline{C} + \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C} + A\overline{B}C + A\overline{B}\overline{C}$ $Y = \overline{A}BC + \overline{A}B\overline{C} + \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C} + A\overline{B}C + A\overline{B}\overline{C}$ <p>This is the canonical form of SOP eqn.</p>	1		
20		2		

Qn. No.	Marks
<p>21. It is the process of using the same carrier frequency in different cells that are geographically separated. Each cell structure is of hexagon shape so that signal covers all the area. The same frequency will be used in two, or more cells which are not adjacent to each other. This would increase the number of subscribers.</p>	1
<p>22. $m_a = \frac{V_m}{V_c} \Rightarrow V_m = m_a V_c$ $V_{max} = V_c + V_m = V_c + m_a V_c = (1+m_a)V_c$ $V_{min} = V_c - V_m = V_c - m_a V_c = (1-m_a)V_c$</p>	1
	1

Qn. No.	PART - C	Marks
---------	----------	-------

I, 23,

$L = 10 \mu H$

Tr. No.	C_1 in μF	C_2 in μF	T in μs	Practical freq. $f = \frac{1}{T}$ in kHz	Theoretical freq. $f = \frac{1}{2\pi\sqrt{LC}}$
1.	0.01	0.02	1.62	617.28 K	616.2 K
2.	0.15	0.22	5.95	168.07 K	168.5 K

Practical frequency = $f = \frac{1}{T} = \dots$ Hz
 Theoretical frequency = $f = \frac{1}{2\pi\sqrt{LC}} = \dots$ Hz
 where $C = \frac{C_1 C_2}{C_1 + C_2}$

Trial no. 1: $\frac{C_1 C_2}{C_1 + C_2} = \frac{0.01 \times 0.02}{0.01 + 0.02} \mu F = \frac{0.02}{3} \mu F$

Theoretical freq. $f_1 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10 \times 10^{-6} \times \frac{0.02}{3} \times 10^{-6}}} = 616.189 \dots$
 $\approx 616.2 \text{ kHz}$

Practical freq. $f_1 = \frac{1}{T_1} = \frac{1}{1.62 \times 10^{-6}} = 617.28 \text{ kHz} \rightarrow \frac{1}{2}$

Trial no. 2: $\frac{C_1 C_2}{C_1 + C_2} = \frac{0.15 \times 0.22}{0.15 + 0.22} \mu F = \frac{3.3}{37} \times 10^{-6}$

Theoretical $f_2 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10 \times 10^{-6} \times \frac{3.3}{37} \times 10^{-6}}} = 168.466 \dots$
 $\approx 168.5 \text{ kHz}$

Practical $f_2 = \frac{1}{T_2} = \frac{1}{5.95 \times 10^{-6}} = 168.1 \text{ kHz} \rightarrow \frac{1}{2}$

Qn. No.

Marks

OR,

$V_i = 0.25V$

Trial No.	R_i in $k\Omega$	R_f in $k\Omega$	V_o in V	Practical gain $A_v = \frac{V_o}{V_i}$	Theoretical gain $A_v = (1 + \frac{R_f}{R_i})$
1	1	10	2.75		
2	47	20	1.314		

Practical gain $= A_v = \frac{V_o}{V_i}$

Theoretical gain $= A_v = 1 + \frac{R_f}{R_i}$

1

Total 1st Pr. gain $A_v = \frac{V_o}{V_i} = \frac{2.75}{0.25} = 11.09$

The gain $A_v = 1 + \frac{R_f}{R_i} = 1 + \frac{10}{1} = 11$

1/2

Trial 2: Pr. gain $A_v = \frac{V_o}{V_i} = \frac{1.314}{0.25} = 5.256$

The gain $A_v = 1 + \frac{R_f}{R_i} = 1 + \frac{20}{47} = 5.255$

1/2

II.

24. Cascading necessity

$A_v \Rightarrow \frac{V_o}{V_i} = \frac{2.5}{20 \times 10^{-3}} = 125$

$G = 20 \log A_v = 20 \log 125 = 20 \times 2.0969$

$= 41.938 \text{ dB}$

1
1
1
1

Qn. No.		Marks
25.	Any two comparisons (each carries 2m)	4
26.	$V_2 = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{12 \times 5 \times 10^3}{(27 + 5) \times 10^3} = 1.875 \text{ V}$	1
/	$I_E = \frac{V_2 - V_{BE}}{R_E} = \frac{1.875 - 0.3}{1 \times 10^3} = 1.575 \text{ mA}$	1
/	$r_o' = \frac{52 \text{ mV}}{I_E} = \frac{52 \times 10^{-3}}{1.575 \times 10^{-3}} = 33.02 \Omega$	1
/	$A_v = \frac{-R_C \parallel R_L}{r_o'} = \frac{-(2.7 \parallel 15) \times 10^3}{33.02} = -53.096$	1
/	$\beta_{r_o'} = 100 \times 33.02 = 3.302 \text{ k}\Omega$	1
/	$Z_{in} = R_1 \parallel R_2 \parallel \beta_{r_o'}$ $= 27 \parallel 15 \parallel 3.302 \text{ k}\Omega$ $= 1.852 \text{ k}\Omega$	1
27.	Block diagram Arriving at the expression	1
/	$A_v = \frac{A}{1 + AB}$	3
28.	$f = \frac{1}{2\pi RC}$	1
/	$= \frac{0.1591}{2 \times 3.142 \times 1 \times 10^3 \times 0.1 \times 10^{-6}}$	1
/	$= \frac{0.1591}{10^{-4}}$ $f = 1591 \text{ Hz}$	1

Qn. No.		Marks
29	$V_{FM} = 100 \sin[18\pi \times 10^7 t + 6 \sin \pi \times 10^4 t]$ $V_{FM} = V_c \sin[2\pi f_c t + m_f \sin 2\pi f_m t]$ <p>Comparing $m_f = 6$, $2\pi f_m = \pi \times 10^4 \Rightarrow f_m = 5 \text{ kHz}$</p> $2\pi f_c = 18\pi \times 10^7 \Rightarrow f_c = 90 \text{ MHz}$ $\Delta f = m_f f_m = 6 \times 5 \times 10^3 \Rightarrow \Delta f = 30 \text{ kHz}$ $\% m_f = \frac{\Delta f_{max}}{\Delta f} \times 100 = \frac{75 \times 10^3}{30 \times 10^3} \times 100 = 250\%$ <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $m_f = 6$, $f_m = 5 \text{ kHz}$, $f_c = 90 \text{ MHz}$, $\Delta f = 30 \text{ kHz}$ $\% m_f = 250\%$ </div>	<p>1</p> <p>1</p> <p>1</p> <p>1</p>
30	<p>Block diagram</p> <p>Explanation</p>	<p>2</p> <p>2</p>
31	<p>Full adder using HA</p> $\text{Sum} = A \oplus B = \overline{A}B + A\overline{B}$ $\text{Carry} = AB$	<p>2</p> <p>1</p> <p>1</p>
PART - D		
I.	<p>32. Pinout diagram of IC 7400</p> <p>Verification of TT with NAND equivalent ckt.</p> <p style="margin-left: 40px;">NOT</p> <p style="margin-left: 40px;">OR</p> <p style="margin-left: 40px;">AND</p> <p style="margin-left: 40px;">XOR</p> <p style="margin-left: 40px;">OR</p>	<p>1</p> <p>1</p> <p>1</p> <p>1</p> <p>2</p>

Qn. No.		Marks
	Pinout diagram of IC 741	1
	Circuit diagram	1
	Tabular column	1
	output equation	1
	Explanation (procedure)	2
II.		
33a)	Circuit diagram	1
	Explanation of stabilization	2
	Equation $I_E \approx I_C$, $V_{CE} = V_{CC} - I_C(R_C + R_E)$	1
	$V_E = V_{BE} + I_E R_E = V_{BE} + I_C R_E$	1
b)	$R_i = \frac{\Delta V_i}{\Delta I_B} = \frac{\Delta V_{BE}}{\Delta I_B} = \frac{0.75 - 0.70}{(30 - 5) \times 10^{-6}}$	1
	$R_i = \frac{0.05}{25 \times 10^{-6}} = 2 \text{ k}\Omega$	1
34.	Circuit diagram	1
	waveforms	1
	Explanation, it working during the half cycle	2
	it working during the half cycle	2
35a)	Circuit diagram	1
	Arriving at the equation	3
	$V_o = -R_C \frac{dI_i}{dt}$	

Qn. No.		Marks
b.		2
36.a)	<p>Circuit diagram</p> <p>Equation — $f = \frac{1}{2\pi(L_1 + L_2)C}$</p>	1
	<p>Explanation</p>	2
b)	<p>Two disadvantages</p> <p>Two disadvantages</p>	2
37.a)	<p>Derivation of power relations.</p> $P_t = P_c(1 + m_a^2)$ $P_{SB} = P_c \frac{m_a}{2}$ $P_{SB} = P_t \left(\frac{m_a^2}{2 + m_a^2} \right)$	2
	<p>b) Definition of — signal to noise ratio</p>	1
	<p>— Fidelity</p>	1
38.	<p>Circuit diagram of MSFF</p> <p>working</p> <p>Truth table</p>	2

Qn. No.		Marks
39. a)	K-map	1
	$Y = \bar{C} + \bar{B} + \bar{D}$	
	Entering 0s, 1s & Xs in different cells of K-map	1
	Proper grouping	1
	Final equation $Y = \bar{C} + \bar{B} + \bar{D}$	1
	NAND gate equivalent ckt 	2
Qn.	Block diagram of monochrome TV receiver	3
	Function of each block	3