



**GOVERNMENT OF KARNATAKA
KARNATAKA STATE PRE-UNIVERSITY EDUCATION EXAMINATION BOARD
II YEAR P.U.C. EXAMINATION OF**

Answer Book Sl. No.
1946835

MARCH 2013

Register No. of the Candidate
3 8 3 4 6 7

MAIN ANSWER BOOK

Please read the instructions overleaf before filling in

Subject Code : 40

Subject : Electronics

Sl. No. of Additional answer sheets used	No. of pages used in		Total No. of Pages used
	Main Answer book	Addnl. answer book/s	
1. 5314228	14	6	20
2. 5317783			
3.	Certified that the entries made above by the Candidate are found to be correct.		
4.			
5.			
6.			
7.			
8.	Signature of the Invigilator with date <i>[Signature]</i> 14/3/13		

FOR THE USE OF EXAMINERS ONLY											Total Marks
Part	Marks awarded										
	1	2	3	4	5	6	7	8	9	10	10
	11	12	13	14	15	16	17	18	19	20	
	21	22	23	24	25	26	27	28	29	30	16
	31	32	33	34	35	36	37	38	39	40	
	41	42	43	44	45	46	47	48	49	50	28
	51	52	53	54	55	56	57	58	59	60	
	61	62	63	64	65	66	67	68	69	70	36
	71	72	73	74	75	76	77	78	79	80	

Grand Total in Words	Ninety only	Grand Total in Figures	90
-----------------------------	-------------	-------------------------------	----

Signature of the Dy. Chief Examiner with date
[Signature]
Code No. of D.E.E. 3007
BHE

Signature of the Reviewer with date
[Signature]
Code No. 3009

Signature of the Assistant Examiner with date
[Signature] 07/09/13
Code No. of A.E. 3011
ELE



INSTRUCTIONS TO CANDIDATES

1. Write your register number Correctly on the space provided on the Facing Sheet of the Answer book and the top left side of Additional answer sheets. Over writing should be attested by the Room Invigilator.
2. Write answers in both sides of the sheet using BLUE/BLACK ink or ball point pen.
3. Obtain Additional Sheets, Graph Sheets, Mathematical table from the Invigilator if required. Enter the serial numbers of all the Additional sheets used.
4. Intimate disorders if any, in the Main Answer book/ Additional sheets to the invigilator.
5. Indicate the Correct question number in the margin.
6. Obtain the permission of the Invigilator for change of PEN / INK.
7. All rough work should be made on a particular page with the heading ROUGH WORK and cross it.
8. Do not write in the margin and leave any page UNUSED except at the end of answers.
9. No Candidate is permitted to leave the examination hall within 30 minutes from the commencement of the examination. Any candidate who leaves after 30 minutes will not be allowed again to the examination hall.
10. If you want to make any request to the Room Invigilator, just stand up to attract his / her attention. Do not shout or leave your place. The invigilator will come to you.
11. During the examination if the candidate wants to go out, for urination etc., same may be informed to the invigilator. While going out, the Answer paper, Question paper etc., should be handed over to the Room Invigilator for safe custody.
12. After completion, just stand up & inform the same to the Room Invigilator who in turn will collect the papers and gets your signature on the diary maintained by the Invigilator.
13. The following misdeeds will attract disciplinary actions and criminal prosecution.
 - a) Breach of silence.
 - b) Use of books, notes, manuscripts, etc.. pertaining to the subject in the examination hall.
 - c) Talking or signalling to other Candidates.
 - d) Candidates copying from the answer books of the other candidates or from other source.
 - e) Sending of answer books or additional sheets or question paper out of the examination hall.
 - f) Impersonation.
 - g) Taking the answer books or additional sheets received for writing the answers out of the examination hall during or after the examination.
 - h) Tearing or insertion to the answer books and the additional sheets.
 - i) Writing an appeal or request to the valuator in the answer book.
 - j) Mobile Phones, Pagers are strictly prohibited in the Examination Hall.
 - k) Simple calculators can be used. Scientific calculators allowed only for Statistics paper.
14. After completion of writing, Count the No. of pages used and fill the columns provided on the facing sheet of the main answer book.
15. Candidates suffering from infectious diseases are not allowed to sit in the examination hall.

Part A.

1. Arrow mark indicates conventional direction of current through transistor.

2. V_{CC} amplifier

3. Distortion decreases

4. Output voltage is zero.

5. RC oscillators

6. It is the distance between last ground wave reception to first sky wave reception.

$$7. m_a = \frac{V_{max} - V_{min}}{V_{max} + V_{min}}$$

8. Output is zero. '1' [Output is one]

9. 010100110100 in excess-3

10. It is a ~~st~~ system that records and retrieves audio signals and plays announcement to callers.

11 $\alpha = 0.98, I_C = 5mA$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$= \frac{0.98}{1-0.98}$$

$$= 49$$


$$\beta = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta}$$

$$= \frac{5 \times 10^{-3}}{49}$$

$$= 102.04 \mu A$$


12

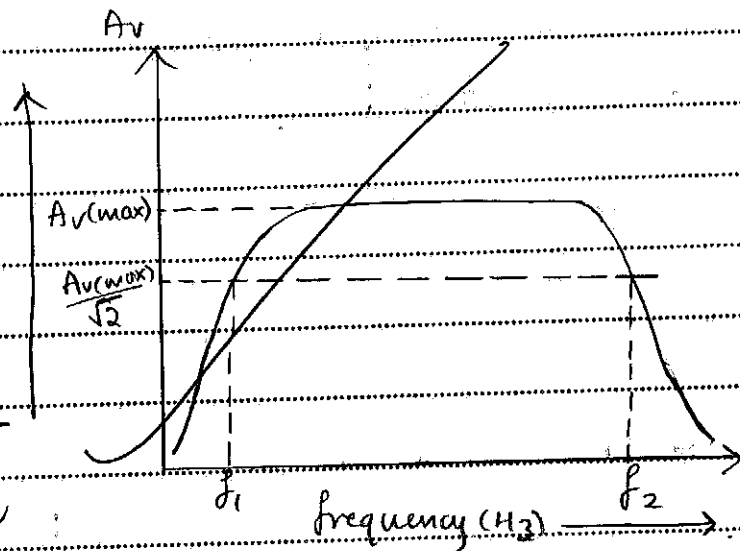

$$\text{Bandwidth} = (f_2 - f_1) \text{ Hz}$$

04

13

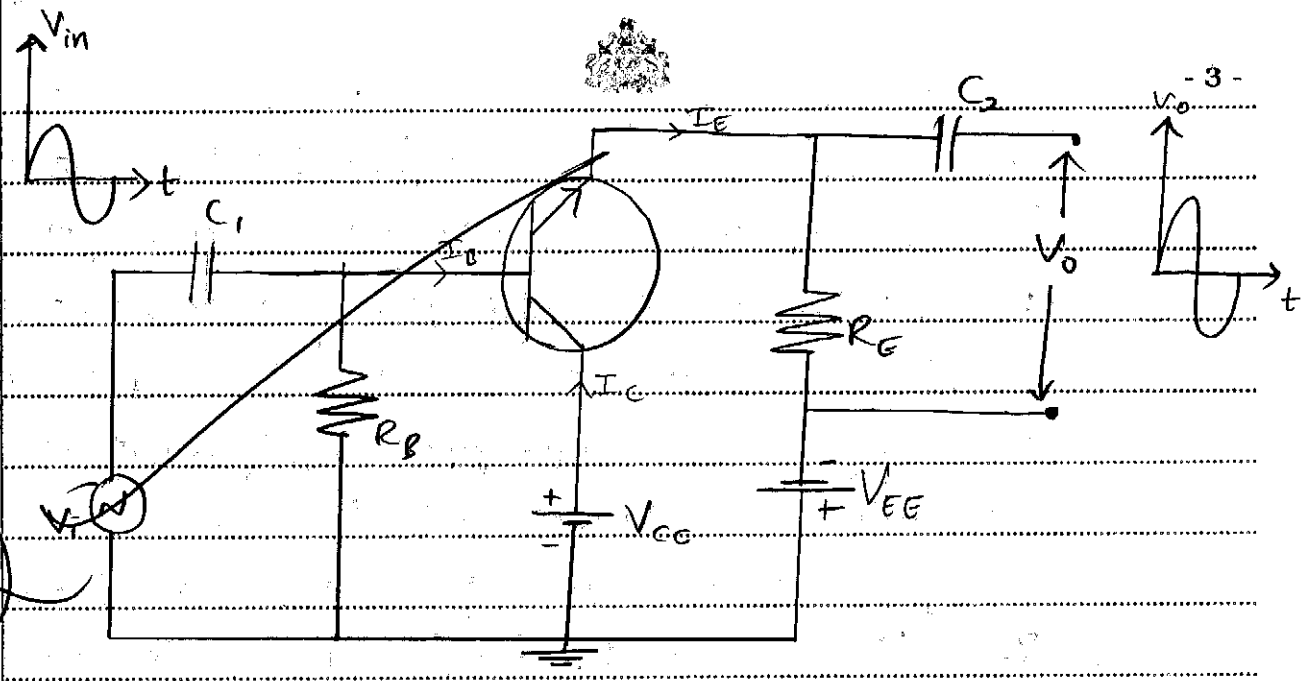

14

Positive feedback

Negative feedback


- 1) Feedback signal is in phase with input signal.
- 2) Gain increases with positive feedback
- 3) Also called regenerative feedback

- 1) Feedback signal is out of phase with input signal.
- 2) Gain decreases with negative feedback
- 3) Also called degenerative feedback

15 Applications of comparator ->

- 1) Schmitt Trigger
- 2) Digital Interfacing

16

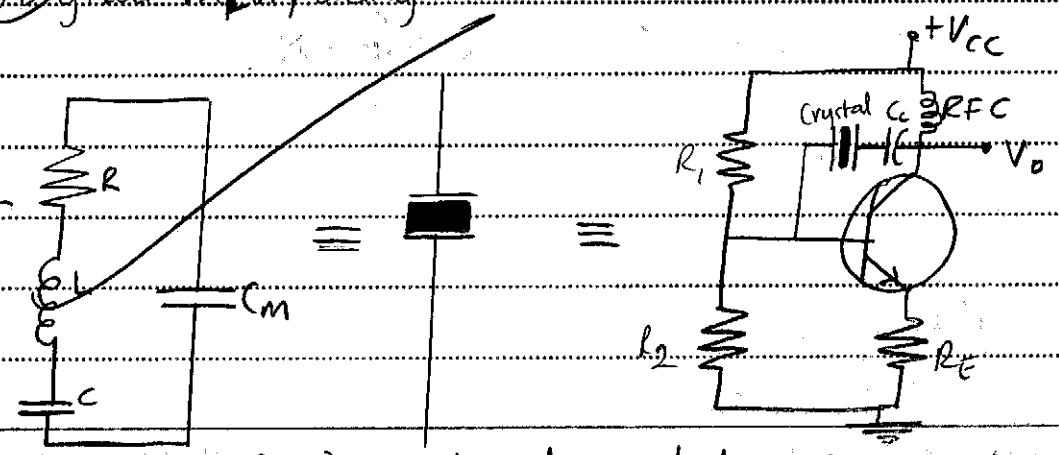

08

ಇದು ಮೂಲಕ ಸಿಕ್ಯಲಿ ಕ್ರಿಸ್ಟಾಲ್ ಸಿಕ್ಯಲಿ ಸಿಕ್ಯಲಿ circuit symbol and equivalent circuit of crystal. ಎರಡನೇ ವಿಷಯ ಪರಿಚ್ಛೇದ - ಮಾರ್ಚ್ 2013


17 Sky waves are transmitted from Earth and directly from transmitter and wave returns back getting reflected by ionospheric layers of Earth. Amount of reflection or refraction of transmitted wave depends on density of ionosphere layer, frequency of wave and angle at which it is incident on that layer.

Space waves consists of 2 components TR and TER.


TR is transmitted directly from transmitter to receiver.

TER component travels along the Earth. It requires good line of sight conditions.

20

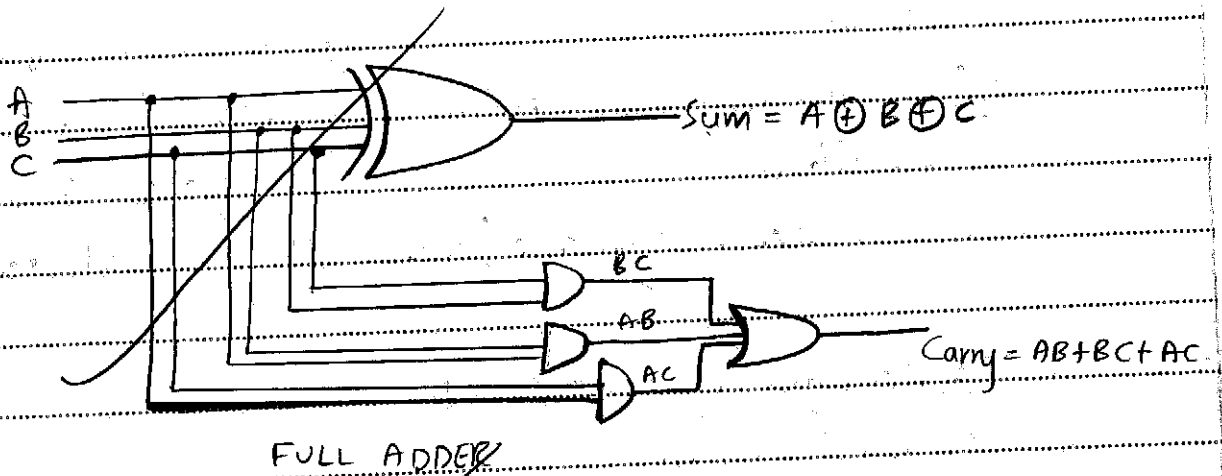

21 Truth table is of XNOR gate.

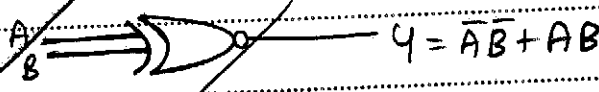

- 22
- 1) Frequency reuse
 - 2) Cell splitting

06

ಪ್ರತಿ ಪುಟದ ಒಟ್ಟು ಅಂಕಗಳು

(1) I

$V_i = 0.5V$

23

Sl.No.	$R_i(k\Omega)$	$R_f(k\Omega)$	$V_o(volt)$	Voltage gain	
				Theoretical $A_v = 1 + \frac{R_f}{R_i}$	Practical $A_v = \frac{V_o}{V_i}$
1	2.2	8.2	2.36	4.727	4.72
2	1.2	5.6	2.83	5.666	5.66

Calculation:-

Experimental:- 1) $A_v = \frac{V_o}{V_i} = \frac{2.36}{0.5} = \underline{\underline{4.72}}$

2) $A_v = \frac{V_o}{V_i} = \frac{2.83}{0.5} = \underline{\underline{5.66}}$

4

Theoretical:- 1) $A_v = 1 + \frac{R_f}{R_i} = 1 + \frac{8.2 \times 10^3}{2.2 \times 10^3} = 3.727 + 1 = \underline{\underline{4.727}}$

2) $A_v = 1 + \frac{R_f}{R_i} = 1 + \frac{5.6 \times 10^3}{1.2 \times 10^3} = \underline{\underline{5.666}}$


II

24

$$V_B = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$= \frac{18 \times 12 \times 10^3}{(47 + 12) \times 10^3}$$

$$= \underline{\underline{3.661V}}$$

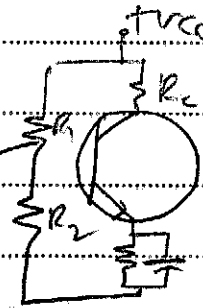

$$I_E = \frac{V_B - V_{BE}}{R_E} = \frac{3.661 - 0.7}{1 \times 10^3} = \underline{\underline{2.961mA}}$$

04

$$r_e = \frac{52 \times 10^{-3} \text{ V}}{2.961 \times 10^{-3} \text{ A}} \quad \left[r_e = \frac{59 \text{ mV}}{I_E} \right]$$

$$= 17.561 \Omega$$

Input base resistance = $R_{in}(\text{base}) = \beta r_e$

$$= 100 \times 17.561$$

$$= 1.756 \text{ k}\Omega$$


Voltage gain = $A_v = \frac{r_o}{r_e} = \frac{R_c \parallel R_L}{r_e} = 141.29$

$R_c \parallel R_L = \frac{R_c R_L}{R_c + R_L} = \frac{3.3 \times 10^3 \times 10 \times 10^3}{13.3 \times 10^3} = 2.481 \text{ k}\Omega$

$A_v = \frac{r_o}{r_e} = \frac{2.481}{17.561} = 0.141 \times 10^3$

$$= 141.29$$

125

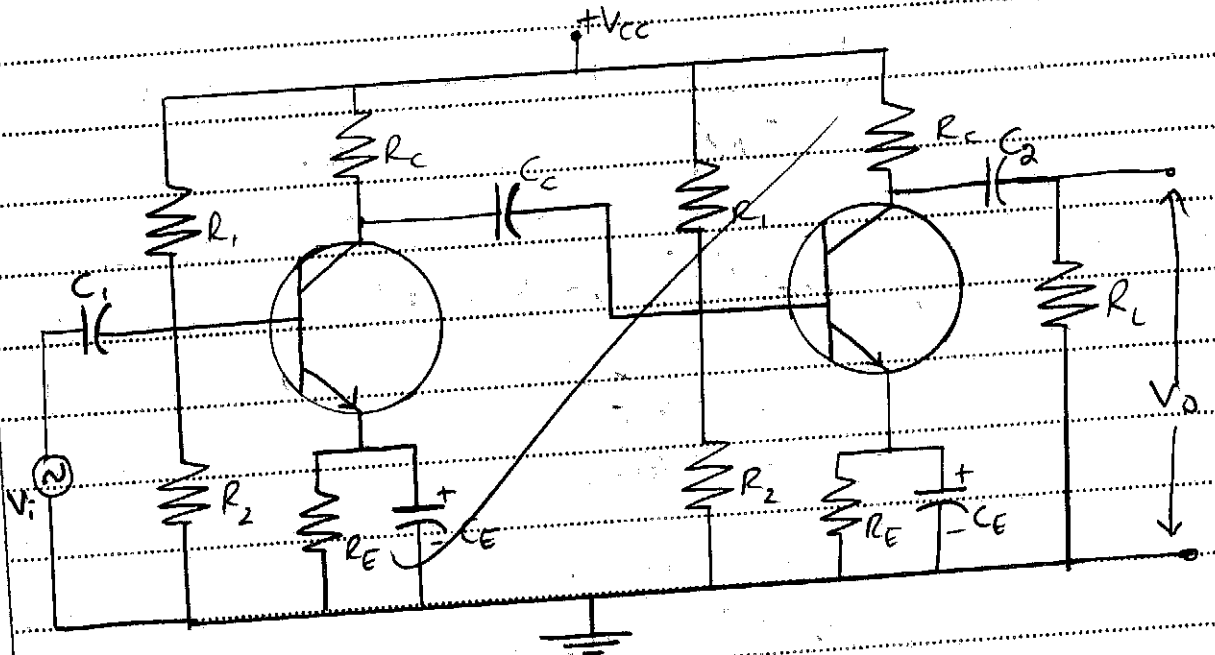

RC-coupled amplifier.

04/ ಪ್ರತಿ ಪುಟದ ಮೇಲ್ಭಾಗ ಅಂಕಗಳು

Advantages - 1) Wide frequency response

2) Low frequency distortion

3) Uses cheap components like resistors and capacitors and overall amplification is more than other amplifiers.

26 $A_v = 150$, $BW_1 = 200\text{KHz}$, $\beta = 0.04$

Gain with negative feedback = $A_{vf} = \frac{A_v}{1+A_v\beta}$

$= \frac{150}{1+150 \times 0.04}$

$= 21.428$


$A_v BW_1 = A_{vf} BW_2$

$BW_2 = \frac{150 \times 200 \times 10^3}{21.428}$

$BW_2 = BW_1(1+A_v\beta)$

$= 1.4\text{MHz}$

27

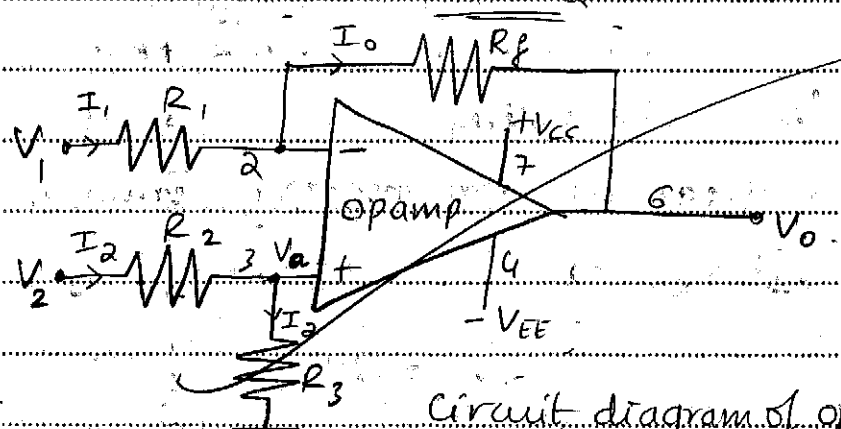

Circuit diagram of op-amp subtractor.

V_1 be the input voltage applied to inverting terminal of op-amp through resistor R_1 and V_2 be the input voltage applied to op-amp through voltage divider circuit consisting of resistors R_2 and R_3 and it is applied to non-inverting terminal.

08

R_f is the feedback resistor which feedbacks portion of output voltage as input to op-amp.

To find the output voltage of op-amp subtractor we have to apply superposition theorem.

$$V_o = V_{o_1} + V_{o_2}$$

V_{o_1} be the output voltage of op-amp with V_1 acting alone and V_2 reduced to zero. Hence the circuit acts as inverting amplifier.

$$V_{o_1} = \left(\frac{-R_f}{R_1} \right) V_1 \quad \text{--- (1)}$$

Let V_{o_2} be the output voltage of op-amp with V_2 acting alone and V_1 reduced to zero. Hence the circuit acts as non-inverting amplifier.

$$V_{o_2} = \left(1 + \frac{R_f}{R_1} \right) V_a$$

$$= \left(1 + \frac{R_f}{R_1} \right) \left(\frac{V_2 R_3}{R_2 + R_3} \right) \quad \text{--- (2)}$$

V_a is the voltage across R_3 , which is actual input voltage at non-inverting terminal.

$$\text{(1) + (2)} \Rightarrow V_o = V_{o_1} + V_{o_2}$$

$$V_o = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{V_2 R_3}{R_2 + R_3} \right) - \frac{R_f}{R_1} V_1$$

If $R_1 = R_2$ & $R_3 = R_f$

$$V_o = \frac{V_2 R_f}{R_1} - \frac{R_f}{R_1} V_1$$

$$V_o = \frac{R_f}{R_1} (V_2 - V_1)$$



(1) If $R_f = R_i$

$$V_o = V_2 - V_1$$

∴ Output of opamp subtractor is equal to difference between two input voltages

28

$$f_o = 15 \times 10^3 \text{ Hz}, \quad C = 0.01 \mu\text{F}, \quad L_1 = 1 \times 10^{-3} \text{ H}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$L = \left(\frac{1}{4\pi^2 f_o^2} \right) \left(\frac{1}{C} \right)$$

$$= \frac{1}{4 \times (2.82)^2 \times (15 \times 10^3)^2 \times (0.01 \times 10^{-6})}$$

$$\approx 11.254 \text{ mH}$$

$$L = L_1 + L_2$$

$$L_2 = L - L_1$$

$$= (11.254 - 1) \times 10^{-3} \text{ H}$$


$$= 10.254 \text{ mH}$$

Part-D


I 32 Aim:- To study the working of op-amp adder.

Components:- IC 741, resistors, dual power supply, variable power supply, voltmeter (DVM)

Circuit diagram:-

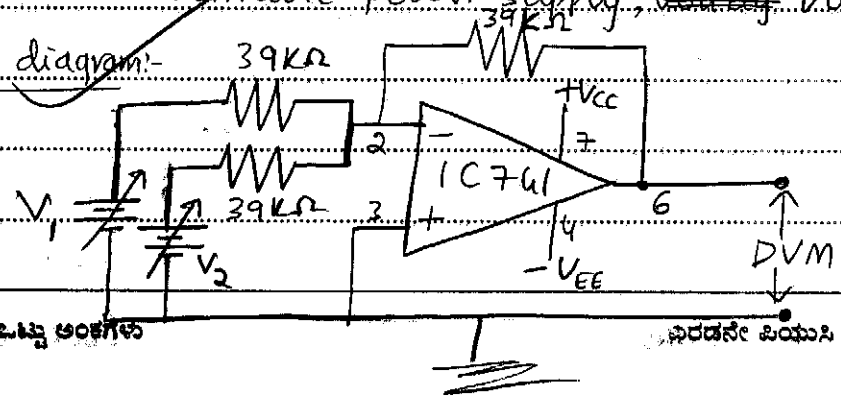

08

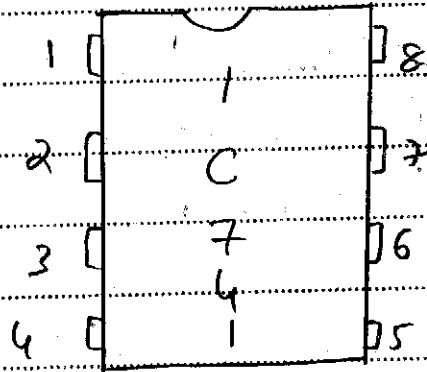

Pin configuration of op-amp

1 and 5 → offset null

2 → Inverting input

3 → non-inverting input

4 → $-V_{EE}$

6 → Output

7 → $+V_{CC}$ 8 → NC

Theory: An operational amplifier is called so because it can perform mathematical operations like addition, subtraction and so on.

In op-amp adder circuit V_1 input voltage is applied through R_1 and V_2 is applied through R_2 to the inverting terminal of op-amp. The non inverting is connected to ground. Terminal 4 is connected to negative power supply $-V_{EE}$ and terminal 7 is connected to positive power supply $+V_{CC}$. Circuit is made as shown in figure.

Procedure: Input voltage V_1 is set to 4V and V_2 is set to 2V and corresponding output voltage is noted. Experiment is repeated for different input combinations and corresponding output is noted. The practical values of output voltage is compared with theoretical values for all the input combinations.


Observations :-

CAUTION: Do not touch the terminals of the op-amp directly.

Trial No.	V_1 (volt)	V_2 (volt)	Output voltage - 11 -	
			Practical V_o (volt)	Theoretical $V_o = -(V_1 + V_2)$ volt
1	4	2		
2	4	-2		
3	-4	2		
4	-4	-2		

Inference :- Theoretical and practical values of output voltage are found to match with each other.

II 33

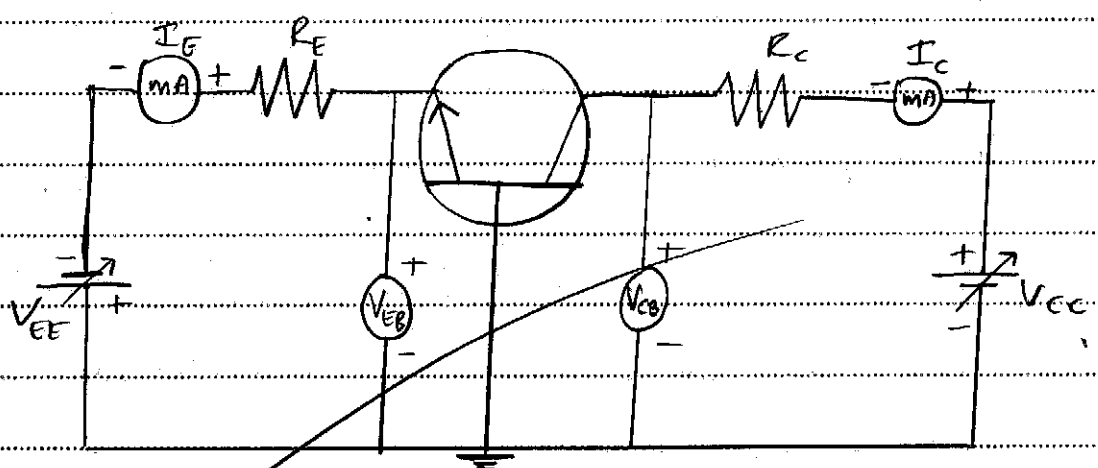


Circuit diagram shows the transistor in CE configuration. Battery V_{EE} forward biases emitter-base junction and battery V_{CC} reverse biases collector-base junction. R_E & R_C are emitter & collector resistors. V_{EB} and V_{CB} can be measured by voltmeters and I_E and I_C is measured through milliammeters.

Input characteristics :- Input characteristic is a plot of emitter current versus emitter to base voltage for a given value of collector to base voltage. By varying V_{CC} , V_{CB} is set to certain value. Now battery V_{EE} is varied

D6

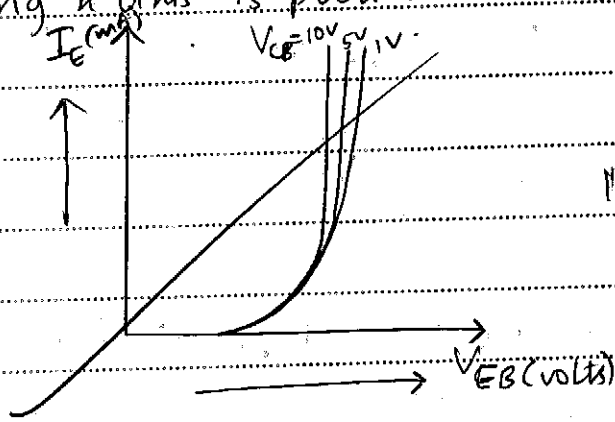to set V_{EB} to particular value and corresponding I_E is noted. A graph of I_E along y axis and V_{EB} along x axis is plotted at constant V_{CB} .




Input resistance = $\frac{\Delta V_{EB}}{\Delta I_E}$
at constant V_{CB}

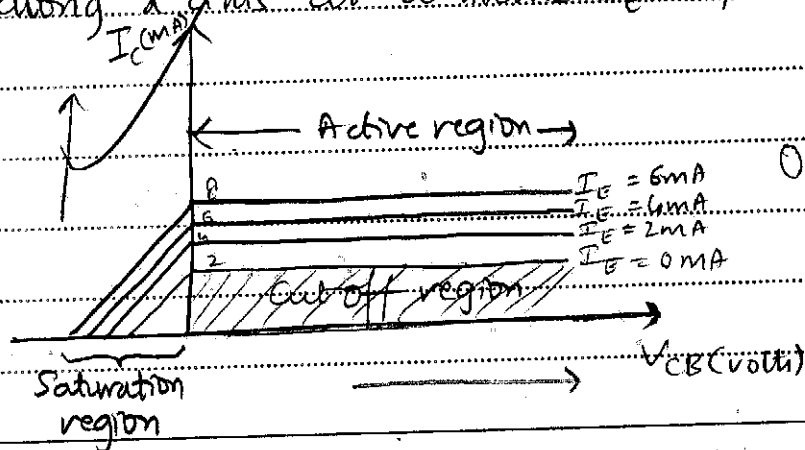- 1) The graph shows that there exist an offset, cut in voltage above which current increases rapidly.
- 2) Input resistance is small.

Output characteristics :- It is a plot of collector current versus collector to base voltage for the given value of emitter current.

By varying V_{EE} , I_E is set to definite value. Now V_{CC} is so varied and V_{CB} is set to particular value and corresponding I_C is noted. A graph of I_C along y axis and V_{CB} along x axis at constant I_E is plotted.




Output resistance = $\frac{\Delta V_{CB}}{\Delta I_C}$
at constant I_E

The graph shows that 1) Even when $I_E = 0$, I_C exists due to reverse saturation current. (cut off region)

2) $V_{CB} = 0$ even then I_C exists. In saturation region I_C is independent of I_E .

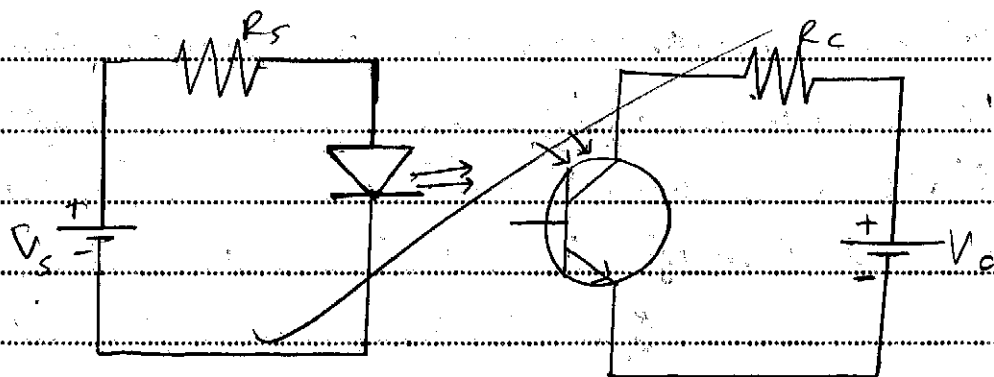3) In Active region I_C is independent of V_{CB} & depends only on I_E

34 a) Current in reverse biased npn transistor (photo transistor) due to thermally generated charge carriers when there is no incident radiation is called as dark current.



opto coupler

Application → 1) It is used in TV remotes

2) In lifts

$$A_v \text{ in dB} = 20 \log \frac{V_o}{V_i}$$


$$\frac{60}{20} = \log \frac{V_o}{40 \times 10^{-3}}$$

$$\text{antilog}(3) = \frac{V_o}{40 \times 10^{-3}}$$

$$V_o = 10^3 \times 40 \times 10^{-3}$$

$$= 40 \text{ V}$$

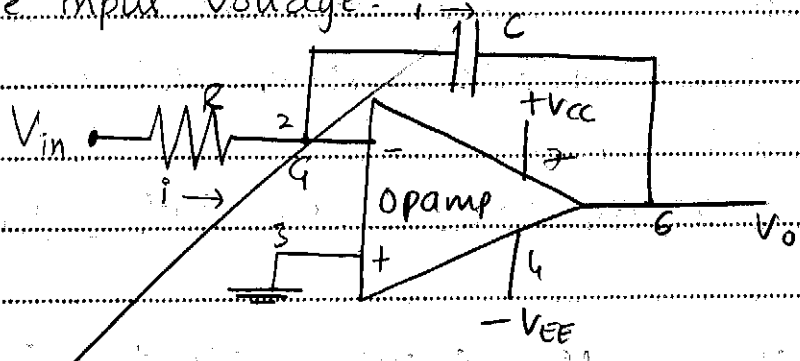35 a) Integrator is device whose output voltage is integral of the input voltage.



Let the input voltage to integrator be applied to inverting terminal through resistor R. Let the capacitor be connected between inverting terminal and output terminal of opamp. Let non inverting terminal of opamp be grounded. Node G is virtual ground. Due to infinite input impedance, current through R and C are same.

$$Q = C(V_G - V_o) \quad V_G = 0V$$

$$Q = -CV_o \quad \text{--- (1)}$$

But $Q = \int i dt$

$$= \int \left(\frac{V_{in} - V_G}{R} \right) dt = \int \frac{V_{in}}{R} dt \quad \text{--- (2)}$$

Substituting (2) in (1)

$$\frac{1}{R} \int V_{in} dt = -CV_o$$

$$V_o = -\frac{1}{RC} \int V_{in} dt$$

The integrator functions properly if RC is equal or greater than T (time constant). Hence output voltage is integral of input voltage.

04




Answer Sheet No. 5314228

Reg. No. 3 8 3 4 6 7

Main Answer Book Sl. No. 1946835

Signature of the Investigator *[Signature]* date

b

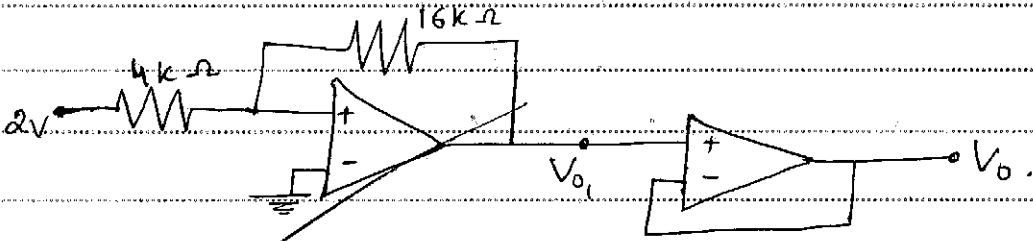

$$V_{o1} = \left(1 + \frac{R_f}{R_i}\right) V_{in}$$


$$= \left(1 + \frac{16 \times 10^3}{4 \times 10^3}\right) 2$$

$$= 10V$$

$$V_o = V_{o1} = 10V \text{ [} \therefore \text{ Buffer amplifier]}$$

2
9 marks

39 a)

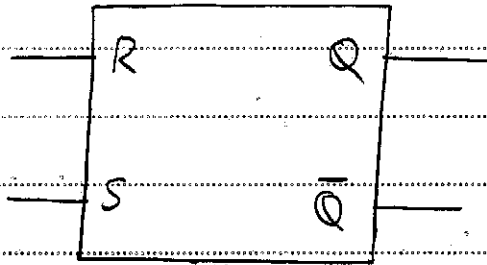


Block diagram of RS flip-flop

R	S	Q	Q̄
0	0	NC	NC
0	1	1	0 (set)
1	0	0	1 (reset)
1	1	Indeterminate condition	

Truth table of RS flip-flop

~~Q = R + S~~

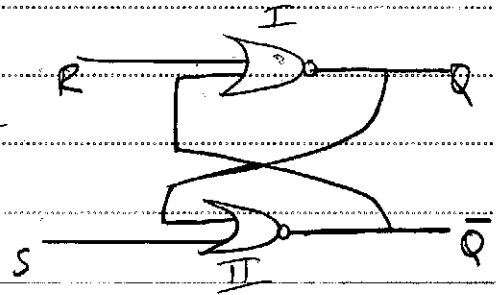RS flip flop can be analysed by using the given diagram. The output of NOR gate is low when any of it's input is high.



02



Case (i): $R = 0, S = 1$, The II ~~and~~^{nor} gate produces zero output as $S = 1$. Hence $\bar{Q} = 0$. Inputs to I nor gate is 0 and 0 to produce high output $Q = 1$. This condition is known as set condition.

Case (ii) $R = 1, S = 0$, Output of I nor gate is zero $Q = 0$. Due to low inputs at II nor gate $\bar{Q} = 1$. This condition is known as reset condition.

Case (iii) $R = 0, S = 0$ let $Q = 0, \bar{Q} = 1$

Input to I nor gate is 0 & 1 to produce low output. Hence II nor gate due to inputs 0 and 0 produces high output i.e. $Q = 0, \bar{Q} = 1$.

Hence there is no change in output.

Case (iv) $R = 0, S = 0$ let $Q = 1, \bar{Q} = 0$.



Input of II nor gate is 0 and 1 to produce low output. Input of I nor gate is 0 and 0 and hence output is high i.e. $Q = 1, \bar{Q} = 0$.

Hence output remains same.


When both $R = 1$ and $S = 1$ both gates produce low output. Hence this input to RS flip flop must be avoided as the output condition is indeterminate.

RS flip flop produces high output is in set condition when $S = 1$ and $R = 0$, It is in reset condition when $S = 0$ and $R = 1$. RS flip flop output remains unchanged when both inputs are zero.

b

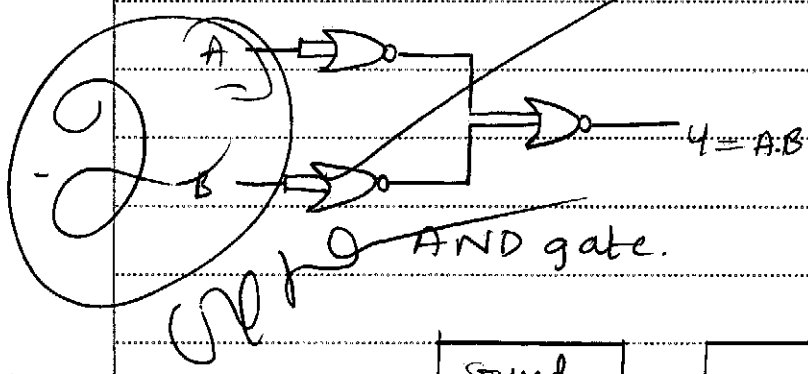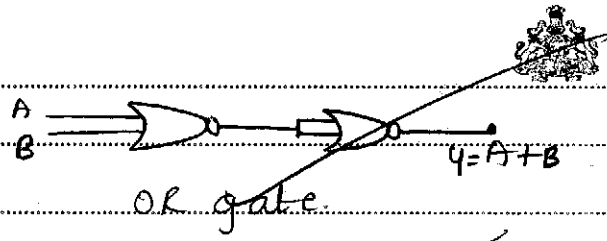

40 a.

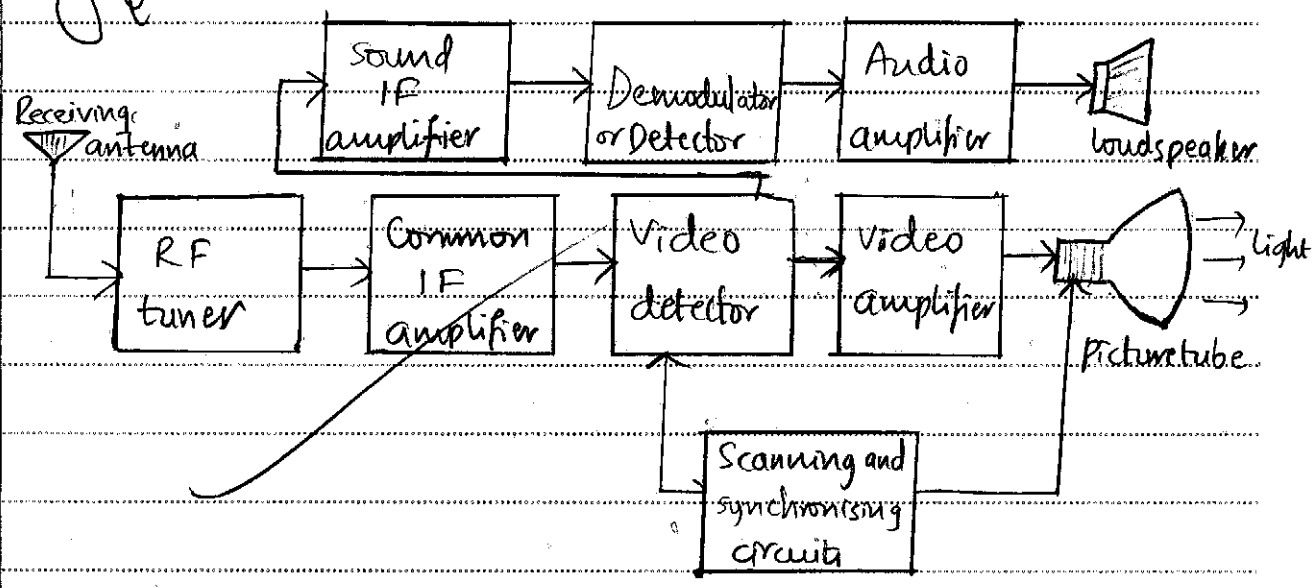

Block diagram of monochrome TV receiver.


b

Uplink signal → signal sent from ~~Earth~~ Earth to satellite is called uplink signal.

Downlink signal → signal sent from satellite to Earth is called downlink signal.

06

a

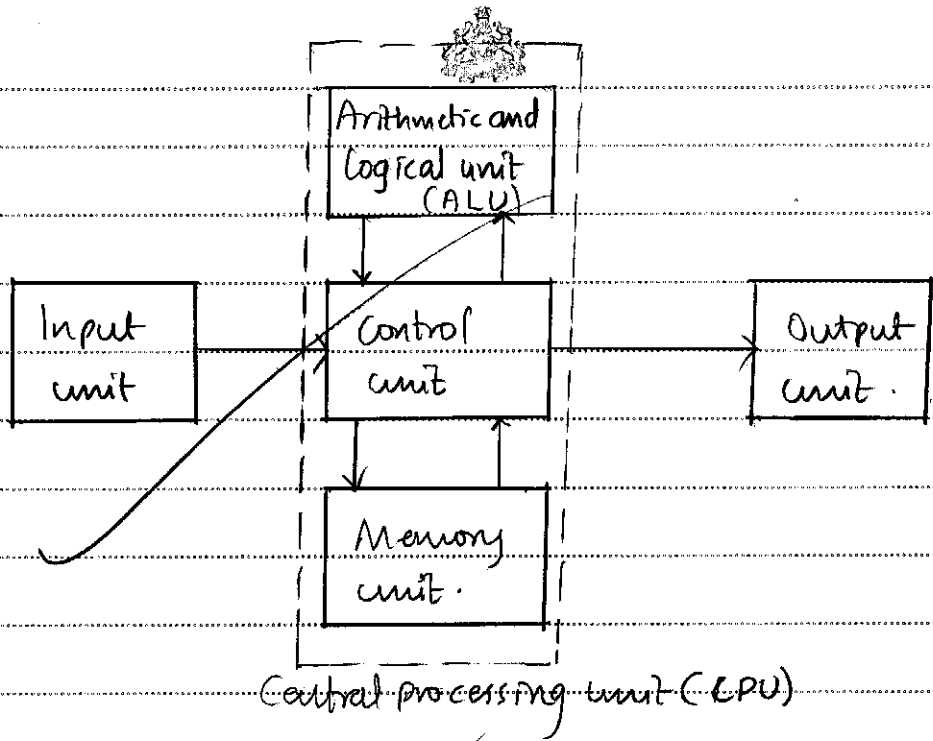

Block diagram of digital computer

ALU → It performs the basic operation like arithmetic operations and also some of the logical operations involved in processing of output.

Memory unit → It stores the information in memory. That is it stores the input and corresponding output generated.

b

$$\begin{aligned}
 Y &= \bar{A}B + B\bar{C} \\
 &= \bar{A}B(C + \bar{C}) + (A + \bar{A})B\bar{C} \\
 &= \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}\bar{C} + \bar{A}B\bar{C} \\
 Y &= \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}\bar{C}
 \end{aligned}$$

06



GOVERNMENT OF KARNATAKA
KARNATAKA STATE PRE-UNIVERSITY EDUCATION EXAMINATION BOARD
II YEAR P.U.C. EXAMINATION - MARCH - 2013
ADDITIONAL ANSWER SHEET

Answer Sheet No. 5317783

Reg. No.

3 8 3 4 6 7

Main Answer Book Sl. No.

1946835

Signature of the Invigilator with date

Part - B

19

Latch

flip flop

1) Output of latch depends or remains same until next input pulse arrives.

1) Output is independent of clock pulse input and output changes with timing of input pulse

Output depends on clock pulse input.

Part - C

31

AB	CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	0	0	1
$\bar{A}B$	1	1	0	0	0
$A\bar{B}$	1	1	0	0	0
AB	1	1	0	0	1


Group 2 (0, 2, 8, 10)

Group 1 (0, 1, 4, 5, 8, 9, 12, 13)

1) There is one octet and 1 quad.

2) There is no pair and no isolated 1's

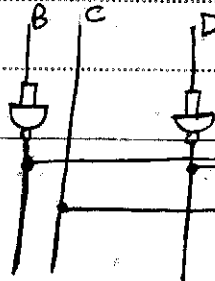3) Output is $Y = \bar{C} + \bar{B}\bar{D}$



ಎರಡನೇ ವಿಭಾಗಕ್ಕೆ ಪರಿಶೀಲನೆ - ಮಾರ್ಚ್ 2013

$Y = \bar{B}\bar{D} + \bar{C}$

ಕ್ಷಮೆ ಪಡೆದ ಒಟ್ಟು ಅಂಕಗಳು

29

30

36a


37 a

Part D

b

b

[Handwritten signature]

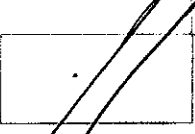

ಪ್ರತಿ ಪುಟದ ಒಟ್ಟು ಅಂಕಗಳು

ಎರಡನೇ ವಿಯುಸಿ ಪರೀಕ್ಷೆ-ಮಾರ್ಚ್ 2013